

Indian Institute of Information Technology, Allahabad

ELECTRONICS AND COMMUNICATION ENGINEERING DEPARTMENT

Course Name: Analog Electronics

EXPERIMENT NO: 2

Objective:

To design and implement the circuit through 741 op-amp IC.

- Inverting amplifier.
- Non-Inverting Amplifier.

Materials/ Component Required :

Digital Storage Oscilloscope (DSO), Function Generator, DC Power Supply, 741 OPAMP IC – 01 No, Resistance (10K – 1 No, 100K – 1 No), Connecting leads

Theory:

- Design for inverting amplifier

The expression for gain is $A_{CL} = -\left(\frac{R_f}{R_i}\right)$

Let amplifier to be designed with a gain of (-10), select input resistance $R_i = 10k\Omega$

Feedback resistance, $R_f = -(A_{CL} \times R_i)$
 $= -(-10 \times 10 \times 10^3) = 100 k\Omega$



- Design for non- inverting amplifier

The expression for gain is $A_{CL} = \left(1 + \frac{R_f}{R_i}\right)$

Let amplifier to be designed with a gain 11 and select $R_i = 10k\Omega$

Feedback resistance, $R_f = (A_{CL} - 1)R_i$
 $= (11 - 1) \times 10 \times 10^3 = 100 k\Omega$

Block Diagram:

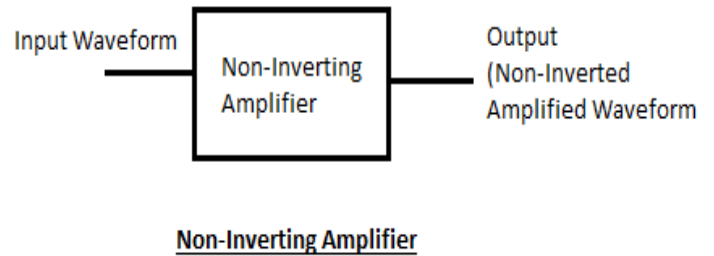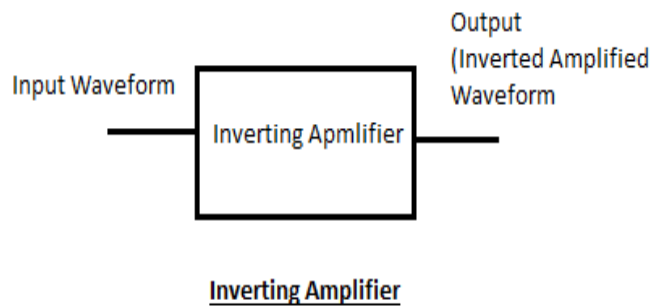

Circuit Diagram:

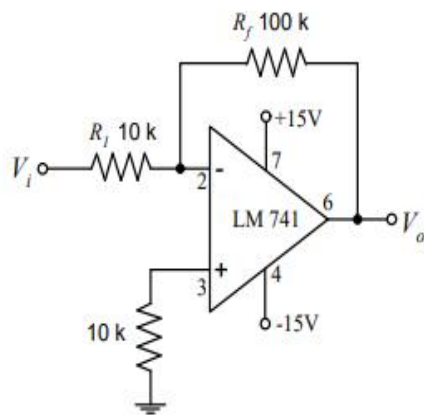


Fig 1. Circuit diagram of inverting amplifier

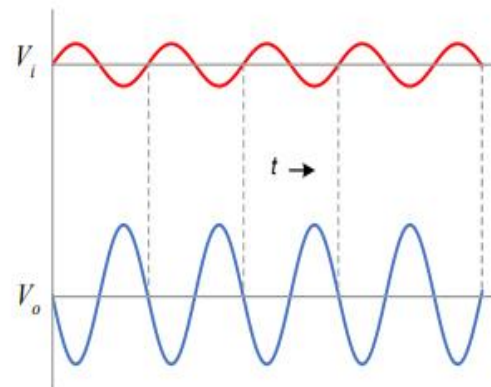


Fig 2. Input and output waveforms of inverting amplifier

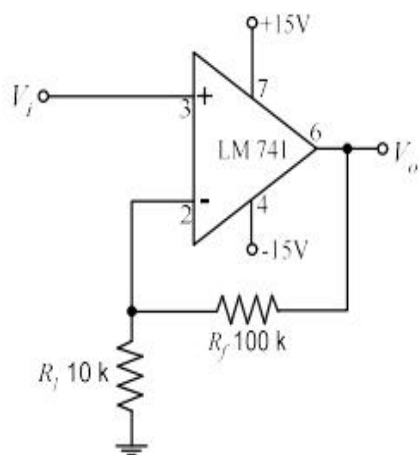


Fig 3. Circuit diagram of non-inverting amplifier

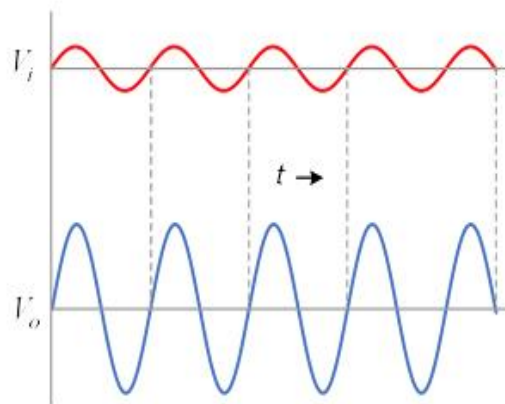


Fig 4. Input and output waveforms of non-inverting amplifier

Observation Table:

For Inverting Amplifier

Input Frequency F (KHz)	Input Voltage Vi (Volts)	Output Voltage Vo (Volts)	Gain A = (Vo/Vi)

For Non-Inverting Amplifier

Input Frequency f (KHz)	Input Voltage Vi (Volts)	Output Voltage Vo (Volts)	Gain A = (Vo/Vi)

Report:

- Define peak inverse voltage (PIV)? And write its value for Full-wave rectifiers?
- What is the mathematical expression for ripple factor?
- Explain how capacitor helps to improve the ripple factor?

Calculation:**Graph:**

Trace the Input and Output waveform observed in CRO/DSO.

Result:

The basic op-amp circuits of inverting & non-inverting amplifiers were designed set up and output waveforms were obtained in a CRO. The gain obtained are

Inverting amplifier: Gain =

Non-inverting amplifier: Gain =

Precautions:

- a) Connections should be verified before clicking run button.
- b) Before switch ON the instruments the connection should be verified.

References:

1. R.A. Gayakward, "Op-Amps and Linear Integrated Circuits" 4th Ed. Pearson-Prentice Hall

