

**Indian Institute of Information Technology, Allahabad**  
**ELECTRONICS AND COMMUNICATION ENGINEERING DEPARTMENT**

Course Name: Analog Electronics Laboratory

**EXPERIMENT NO: 4**

**Objective:**

To design and verify the operation of op-amp as an adder and subtractor.

**Materials/ Component Required:**


S.No	Particulars	Specifications	Quantity
1	Op-amp	μA 741	01
2	Resistors	10Kohm	03
3	Multimeter		01
4	DC Power Supply		01
5	CRO + BNC Probes		01+ 03
6	Connecting Wires		As per use
7	Bread Board		01
8	Power Cords		03

**(a) Summing Amplifier (Inverting)**

**Theory:**

Previously in the inverting operational amplifier, the inverting amplifier has a single input voltage, ( $V_{in}$ ) applied to the inverting input terminal. If we add more input resistors to the input, each equal in value to the original input resistor, ( $R_{in}$ ), this end up with another operational amplifier circuit called a Summing Amplifier, “summing inverter” or even a “voltage adder” circuit as shown below.

**Circuit Diagram:**

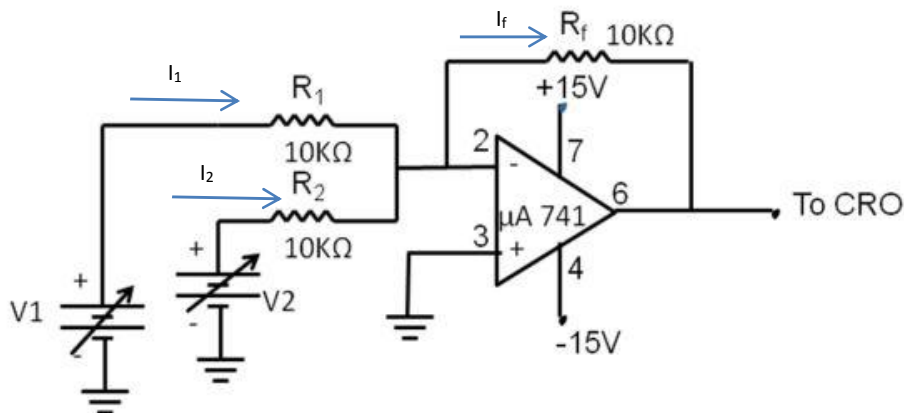

**Design and Calculations:**

From circuit, applying KCL at node 2 along with virtual ground concept at terminal 2 and 3,

$$I_1 + I_2 = I_f \equiv \frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_{out}}{R_f}$$

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \quad \text{This is weighted summing amplifier}$$


$$\text{If } R_1=R_2 \text{ then, } V_{out} = -\frac{R_f}{R_1} (V_1 + V_2) \quad \text{Summing Amplifier}$$

$$\text{If } R_f=R_1 \text{ then, } V_{out} = -(V_1 + V_2) \quad \text{Inverting voltage adder/summing circuit}$$

## (b) Difference Amplifier
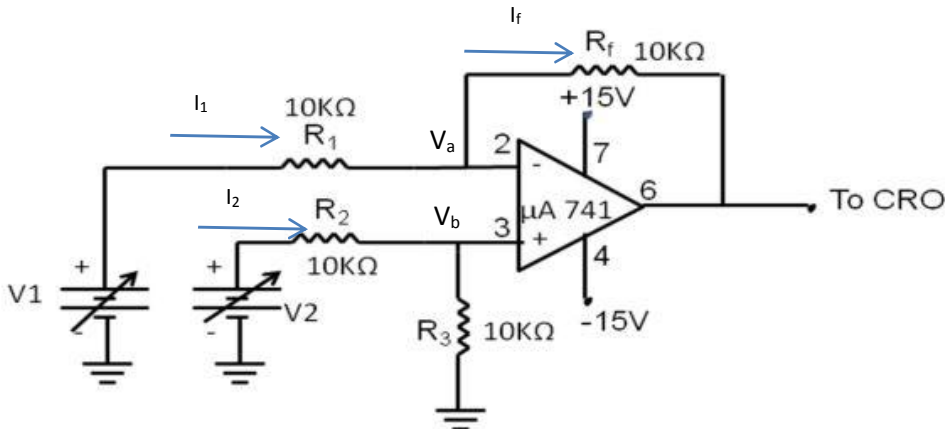
### Theory:

In the previous circuits, only one terminal, inverting or non-inverting, were used as input. If both terminals connected to 2 different signals then the output will provide the difference of the two signals hence known as difference amplifier.



### Design and Calculations:

From Circuit

$$I_1 = \frac{V_1 - V_a}{R_1}, \quad I_2 = \frac{V_2 - V_b}{R_2}, \quad I_f = \frac{V_a - V_{out}}{R_f}$$

Using virtual ground concept:  $V_a = V_b$

$$\text{Through voltage divider rule at non-inverting terminal: } V_b = V_2 \left( \frac{R_3}{R_2 + R_3} \right)$$

Now, applying Superposition theorem:

$$\text{If } V_2=0, \text{ then: } V_{out(a)} = -V_1 \frac{R_f}{R_1}$$

$$\text{If } V_1=0, \text{ then: } V_{out(b)} = V_2 \left( \frac{R_3}{R_2 + R_3} \right) \left( \frac{R_1 + R_f}{R_1} \right)$$

$$V_{out} = V_2 \left( \frac{R_3}{R_2 + R_3} \right) \left( \frac{R_1 + R_f}{R_1} \right) - V_1 \frac{R_f}{R_1}, \quad \text{Weighted Difference Amplifier}$$

If  $R_1=R_2$  and  $R_3=R_f$ , then:

$$V_{out} = \frac{R_3}{R_1} (V_2 - V_1), \quad \text{Difference Amplifier}$$

If all resistances are equal then:  $V_{out} = (V_2 - V_1)$  Subtractor

### Observation Table:

S.No	V <sub>ref</sub> (Volts)	V <sub>i</sub> (Volts)	V <sub>o</sub> (Volts)
1			
2			
3			
4			

**Report:****Result:**

The summing and difference amplifier circuits has been implemented and operation verified accordingly.

**Precautions:**

- a) Connections should be verified before switching on the supply.
- b) The resistance to be chosen should be in proper range and of calculated values.

**References:**

1. [https://www.electronics-tutorials.ws/opamp/opamp\\_4.html](https://www.electronics-tutorials.ws/opamp/opamp_4.html)
2. [https://www.electronics-tutorials.ws/opamp/opamp\\_5.html](https://www.electronics-tutorials.ws/opamp/opamp_5.html)
3. R.A. Gayakward, "Op-Amps and Linear Integrated Circuits" 4<sup>th</sup> Ed. Pearson-Prentice Hall

