

**Indian Institute of Information Technology, Allahabad**  
**ELECTRONICS AND COMMUNICATION ENGINEERING DEPARTMENT**

Course Name: Analog Electronics Laboratory

**EXPERIMENT NO: 9**

**Objective:**

Operating modes of 555 Timer ICs and Working


**Components:**

Components	Quantity	Values
555 Timer ICs		
Resistances	2	3.9 k $\Omega$ , 5.1 k $\Omega$
Capacitors	2	0.1 $\mu$ f, 0.01 $\mu$ f
Power Supply	1	5-9 V
DSO	1	

**Mode of Operations:**

1. Bistable Multivibrator
2. Monostable Multivibrator
3. Astable Multivibrator


**1. Bistable Mode of Operation:**

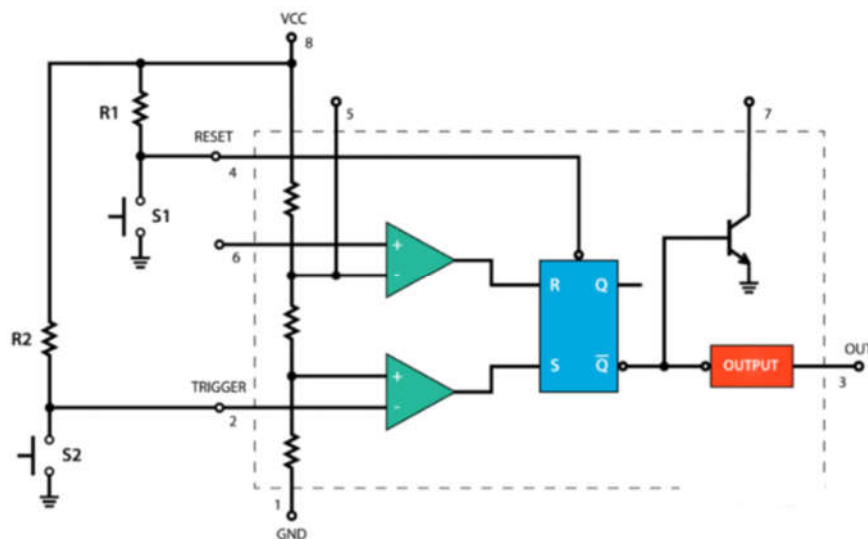

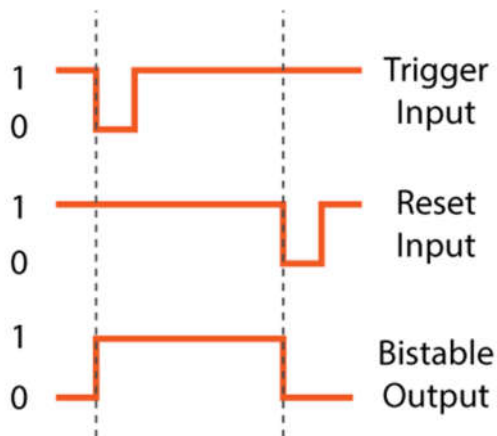
**Working:**


- As per the circuits given above, it needs 2 resistances and 2 input supply either by direct connection or by switches (S1, S2) at pin 4 (Reset) and pin 2 (Trigger)
- Both are connected to  $V_{cc}$  by 2 resistances and hence they remain always high when not connected.

- Initially assuming that the Flip-Flop (FF) is resetted previously hence  $Q=0$  and  $Q_{\text{bar}}=1$  leads to  $\text{Out}=0$ .
- Now, S2 are switched on making pin 2 (Trigger low).
- Lower comparator out =1 (as  $1/3V_{\text{cc}} > 0$ ) and upper comparator out=0 (as pin 6 is disconnected).
- Now the current input to FF is  $(S, R) = (1, 0) \Rightarrow$  Set Condition, making  $(Q, Q_{\text{bar}}) = (1, 0)$  leads to  $\text{Out}=1$ .
- If, the connection from pin2 removed, Lower comparator out = 0, upper comparator out = 0,  $(S, R) = (0, 0)$  i.e. No change condition. Hence even after switching off the input trigger connection, the output value holds,  $\text{Out}=1$ .
- Now, Switch S1 get connected making pin 4 (Reset) low which completely reset the FF leads to  $(Q, Q_{\text{bar}}) = (0, 1) \Rightarrow \text{Out}=0$ .
- The complete waveform is given below.




## 2. Monostable Mode of Operation:

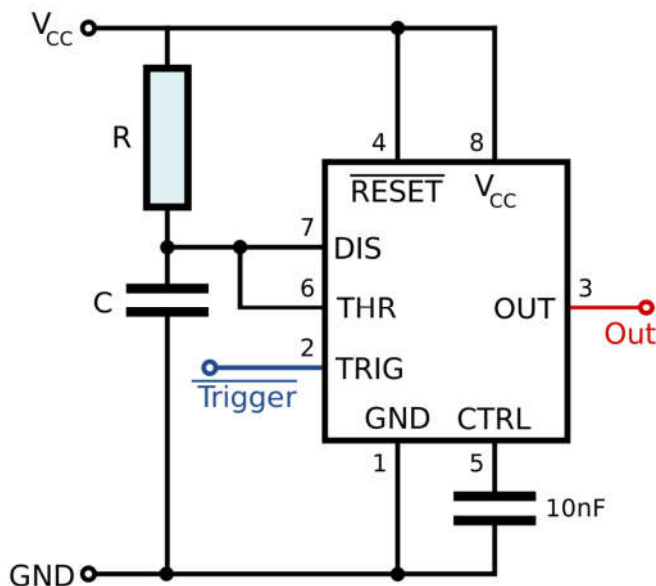


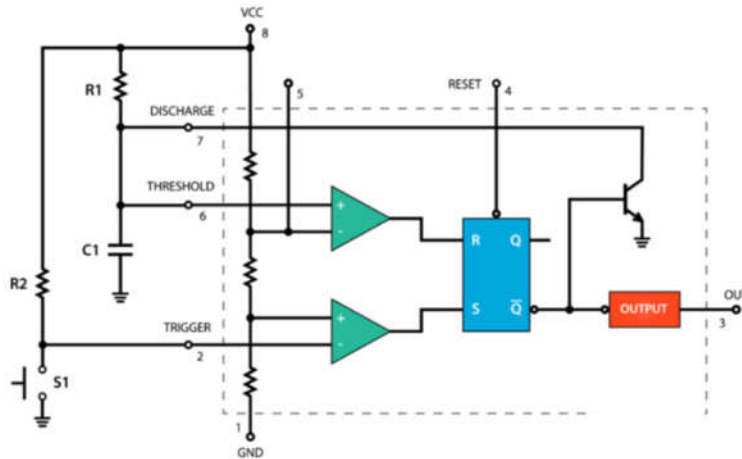

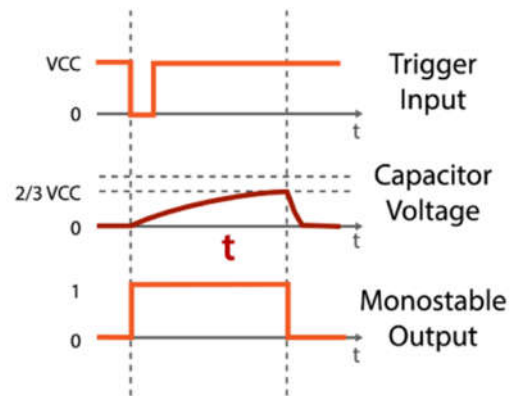
### Working:

- Pin 7 (Discharge) and pin 6 (Threshold) held short circuited and connected to  $V_{cc}$  by resistance R1. Again the same connection is attached to a charging-discharging capacitor C1 with the ground.
- Pin 2 (trigger) is the only controlling input and this input either can be directly given a lower voltage by a power supply (upper diagram) or may be connected to  $V_{cc}$  by a current limiting resistance with switch making ground if on.
- Initially, assuming switch is off and C1 do not holds any charge  $\Rightarrow$  Pin 6=0 and Pin 2= $V_{cc}$  (1).
- Upper comparator out=0 ( $0 < 2/3 V_{cc}$ ) and lower comparator out=0 ( $1/3 V_{cc} < V_{cc}$ )  $\Rightarrow$  (S, R)=(0, 0) i.e. No change condition.
- Assuming, FF is being resetted previously  $\Rightarrow$  (Q,  $Q_{bar}$ )=(0, 1)  $\Rightarrow$  Out=0.
- At the same time,  $Q_{bar}=1$  making the NPN transistor ON which provides the connection between the Pin 7 to ground which in turn provides the least resistance path for both  $V_{cc}$  and discharging the capacitor.
- Now, as soon the switch S1 get connected making Pin 2 (trigger) low  $\Rightarrow$  Lower comparator out switches to=1 ( $0 < 1/3 V_{cc}$ ). The conditions for upper comparator remain same at this time.
- Now (S, R)=(1, 0) Set condition  $\Rightarrow$  (Q,  $Q_{bar}$ )=(1, 0)  $\Rightarrow$  Out=1
- At same time,  $Q_{bar}=0$  switching off the transistor. And hence C1 get connected to  $V_{cc}$  and starts charging via R1 (This charging time depends upon  $R1C1$  factor and on time will be decided by this).
- The capacitor keep charging and reache to  $V_{c1} > 1/3 V_{cc} \Rightarrow$  Lower comparator out = switches to 0 and upper comparator condition still same  $\Rightarrow$  (S, R)=(0, 0) i.e. No change condition hence Out=1.
- Next condition,  $V_{c1} \geq 2/3 V_{cc}$ , Upper comparator output now switches to '1'  $\Rightarrow$  (S, R) = (0, 1) i.e. Reset condition  $\Rightarrow$  (Q,  $Q_{bar}$ )=(0, 1)  $\Rightarrow$  Out=0
- At the same time, NPN transistor switched on and provided the low resistance path to discharge the capacitor.
- The detailed waveform is given below.
- ON time of pulse can be calculated by  $T_{ON} = 1.1 \times R1 \times C1$ .




### 3. Astable Mode of Operation:

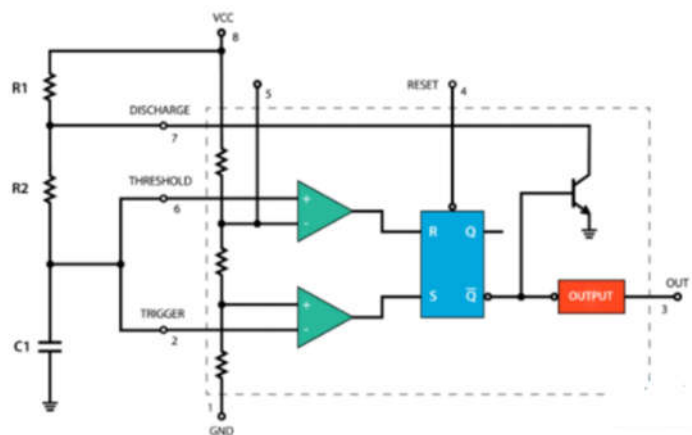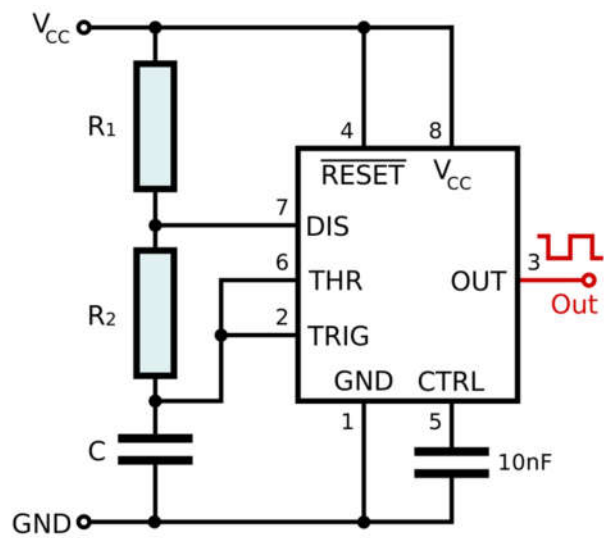

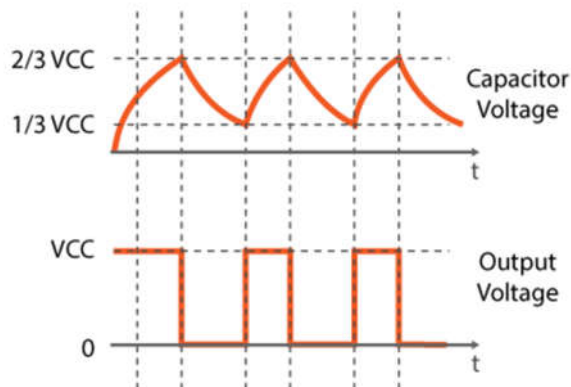**Working:**

- It is also known as free running multivibrator and doesn't have any stable state. It keeps switching between high and low states without any external trigger or input except  $V_{cc}$ .
- Detailed connection is given above.
- Initially, assuming that there is no charge stored in capacitor  $C1 \Rightarrow$  making Pin 6 (Threshold) and Pin 2 (Trigger) low.
- Due to this, Upper comparator out = 0 ( $0 < 2/3V_{cc}$ ) and lower comparator out = 1 ( $1/3V_{cc} > 0$ )  $\Rightarrow (S, R) = (1, 0)$  Set condition  $\Rightarrow (Q, Q_{\bar{bar}}) = (1, 0) \Rightarrow$  Out = 1 (high).
- At the same time,  $Q_{\bar{bar}} = 0$  keeping NPN transistor off  $\Rightarrow$  Pin 7 (Discharge) is disconnected to ground.
- Hence,  $C1$  starts charging via  $R1$  and  $R2$  by  $V_{cc}$  (Charging time depends upon  $(R1+R2) \times C1$ ).
- Now, as  $C1$  is charging,  $V_c$  reaches to  $1/3V_{cc}$  ( $V_c \geq 1/3V_{cc}$ , switching condition of lower comparator) Lower comparator output switches to '0'  $\Rightarrow (S, R) = (0, 0)$  (as upper comparator conditions intact) i.e. No change condition  $\Rightarrow$  Out = 1 (Hold)
- Next  $V_c$  reaches to  $2/3V_{cc}$  ( $V_c \geq 2/3V_{cc}$ , Switching condition of upper comparator), Upper comparator switches to '1'  $\Rightarrow (S, R) = (0, 1)$  (as lower comparator conditions intact) i.e. Reset condition making  $(Q, Q_{\bar{bar}}) = (0, 1) \Rightarrow$  Out = 0.
- At the same time  $Q_{\bar{bar}} = 1$  making NPN transistor ON hence providing a least resistance path to Capacitor  $C1$  to discharge via  $R2$  only (Discharge time depends on  $R2 \times C1$ ).
- As soon as  $V_c < 2/3V_{cc}$ , Upper comparator again switches to '0'  $\Rightarrow (S, R) = (0, 0) \Rightarrow$  Hold condition  $\Rightarrow$  Out = 0.
- On discharging,  $V_c$  again reaches to  $1/3V_{cc}$  ( $V_c \leq 1/3V_{cc}$ ), Lower comparator out = 1  $\Rightarrow (S, R) = (1, 0)$  i.e. Set condition  $\Rightarrow (Q, Q_{\bar{bar}}) = (1, 0) \Rightarrow$  Out = 1.
- At the same instant, NPN become off again, Disconnect to ground. And hence  $C1$  again starts charging.
- The above steps keep repeating between the values of  $1/3V_{cc}$  to  $2/3V_{cc}$ .
- $T_{ON} = 0.693 (R1+R2) \times C1$
- $T_{OFF} = 0.693 R2 \times C1$
- Time period  $T = T_{ON} + T_{OFF} = 0.693 (R1+2R2) \times C1$
- The detailed waveform is given below.



#### References:

1. [https://www.electronics-tutorials.ws/waveforms/555\\_timer.html](https://www.electronics-tutorials.ws/waveforms/555_timer.html)
2. <https://www.jameco.com/Jameco/workshop/TechTip/555-timer-tutorial.html>
3. <https://howtomechatronics.com/how-it-works/electronics/555-timer-ic-working-principle-block-diagram-circuit-schematics/>