

Indian Institute of Information Technology, Allahabad

ELECTRONICS AND COMMUNICATION ENGINEERING DEPARTMENT

Course Name: Electrical Engineering

EXPERIMENT NO: 6

Objective:

To find out the current in single phase AC circuit.


Materials/ Component Required:

Bread board, Digital Multi meter, Resistance, Function generator, Connecting Wires.

Theory:


The root mean square (RMS) is defined as the square root of the mean square (the arithmetic mean of the squares of a set of numbers). RMS value of the function $I(t)$ (current) is the constant current that yields the same power dissipation as the time-averaged power dissipation of the current $I(t)$.

Circuit Diagram:

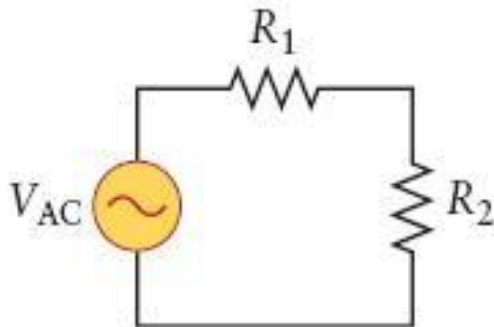

$$RMS\ Value = \sqrt{\frac{1}{T} \int_0^T f(x)^2 dx}$$

Calculation:

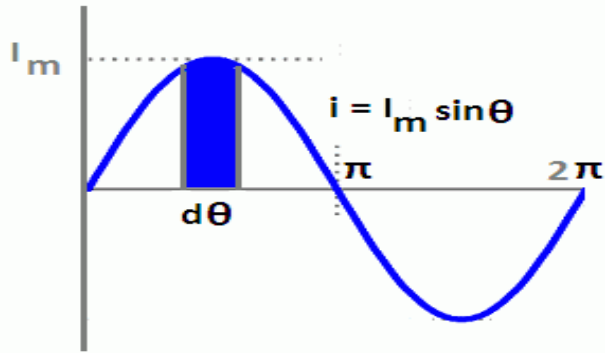

The term *rms* stands for (square) root of the mean of the squares of the instantaneous current values.

$$\begin{aligned} \therefore I_{rms} &= \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 \cdot d\theta} \\ I_{rms}^2 &= \frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta \, d\theta = \frac{I_m^2}{\pi} \int_0^{\pi} \sin^2 \theta \cdot d\theta \\ &= \frac{I_m^2}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) \cdot d\theta = \frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) \cdot d\theta \\ &= \frac{I_m^2}{2\pi} \left[\theta - \frac{1}{2} \sin 2\theta \right]_0^{\pi} \\ &= \frac{I_m^2}{2\pi} \left[\left(\pi - \frac{1}{2} \sin 2\pi \right) - \left(0 - \frac{1}{2} \sin 2 \times 0 \right) \right] \\ &= \frac{I_m^2}{2\pi} | \pi - 0 - 0 + 0 | = \frac{\pi}{2\pi} I_m^2 = \frac{I_m^2}{2} \\ \therefore I_{rms} &= \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m \end{aligned}$$

Result:

Precautions:

- Connections should be verified before clicking run button.
- The resistance to be chosen should be in K ohm range.
- Best performance is being obtained within 50Hz to 1Mhz.