

# Indian Institute of Information Technology, Allahabad

## ELECTRONICS AND COMMUNICATION ENGINEERING DEPARTMENT

### Course Name: Fundamental of Electrical and Electronics

#### EXPERIMENT NO: 11

#### Objective:

To implement and verify reciprocity theorem.


#### Materials/ Component Required :

Bread board, Digital Multimeter, Resistance, DC Power supply, Connecting Wires

#### Theory:

The reciprocity theorem states that if an emf  $E$  in one branch of a reciprocal network produces a current  $I$  in another, then if the emf  $E$  is moved from the first to the second branch, it will cause the same current in the first branch, where the emf has been replaced by a short circuit

#### Circuit Diagram:

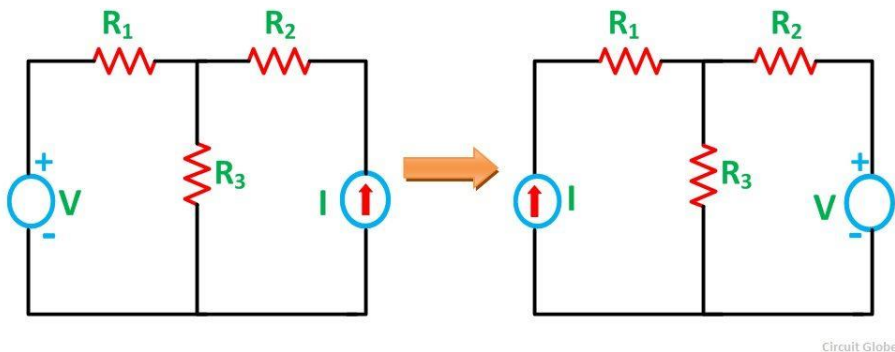

Circuit Globe

#### Observation Table:

Value of current  $I$

Value of voltage  $V$

**Calculation:**

**Result:**

**Precautions:**

- a) Connections should be verified before clicking run button.
- b) The resistance to be chosen should be in Kohm range.
- c) Best performance is being obtained within 50Hz to 1Mhz.